

Design of a Miller compensated Two stage Op-amp with a single-ended output.

Input Stage	nMOS
Load	R=20k $\Omega$ C=5pF


Name- Dushyant

Roll no: 241040022

MVLSI IIT KANPUR





## CHARACTERISATION OF nMOS

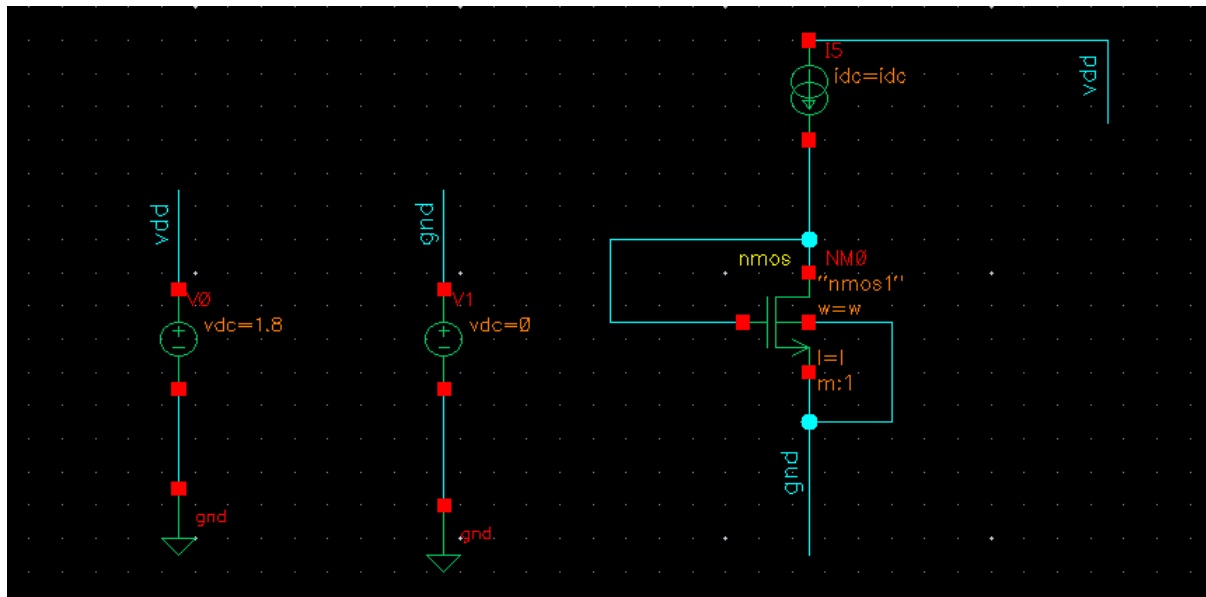


For characterisation of nMOS and pMOS, I varied the  $I_{dc}$  and extracted the parameters such as  $g_m/i_d$ ,  $g_{ds}$ ,  $g_m$ ,  $c_{gg}$ ,  $v_{gs}$ ,  $v_{ds}$ .

- From these parameters I tried to get width independent graphs which are  $(g_m/i_d \text{ vs } i_d/w)$ ,  $(g_m/g_{ds} \text{ vs } i_d/w)$ ,  $(g_{ds}/i_d \text{ vs } i_d/w)$ .
- I have generated these graphs for different lengths.
- The lengths that I have chosen to generate these graphs are. 1.  $L=180\text{nm}$  2.  $L=360\text{nm}$  3.  $L=540\text{nm}$  4.  $L=720\text{nm}$  5.  $L=900\text{nm}$


## Graphs for nMOS

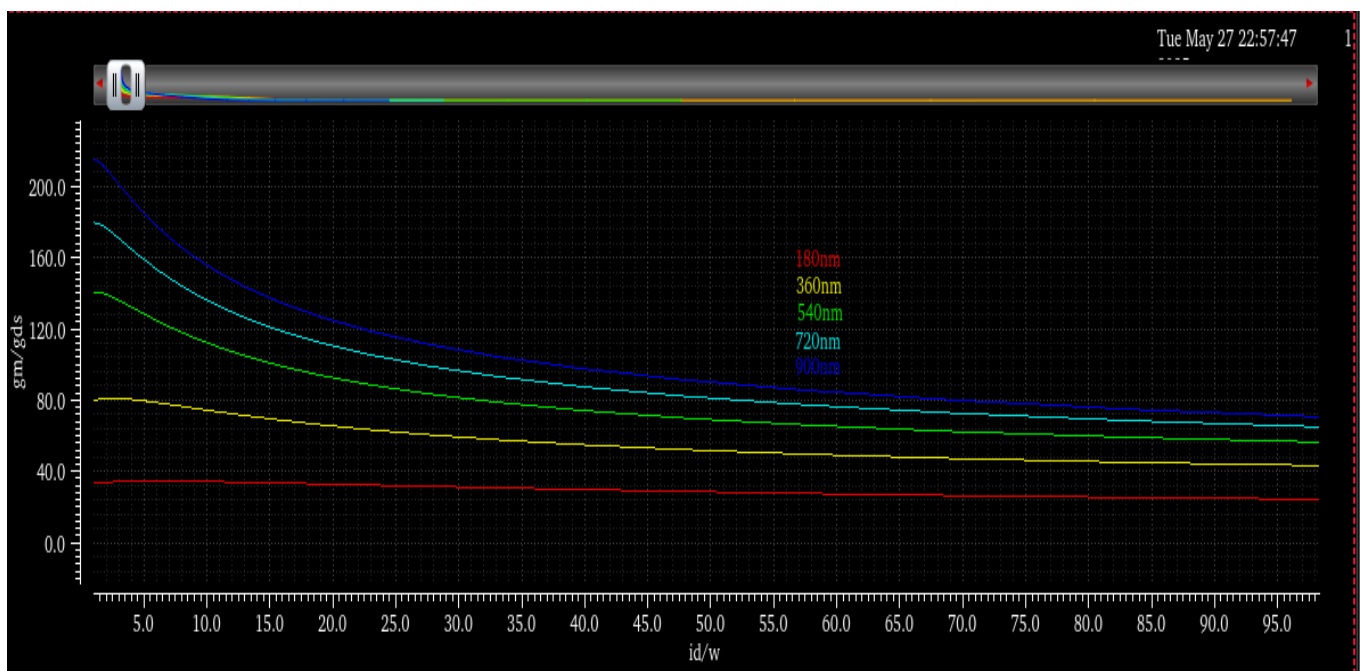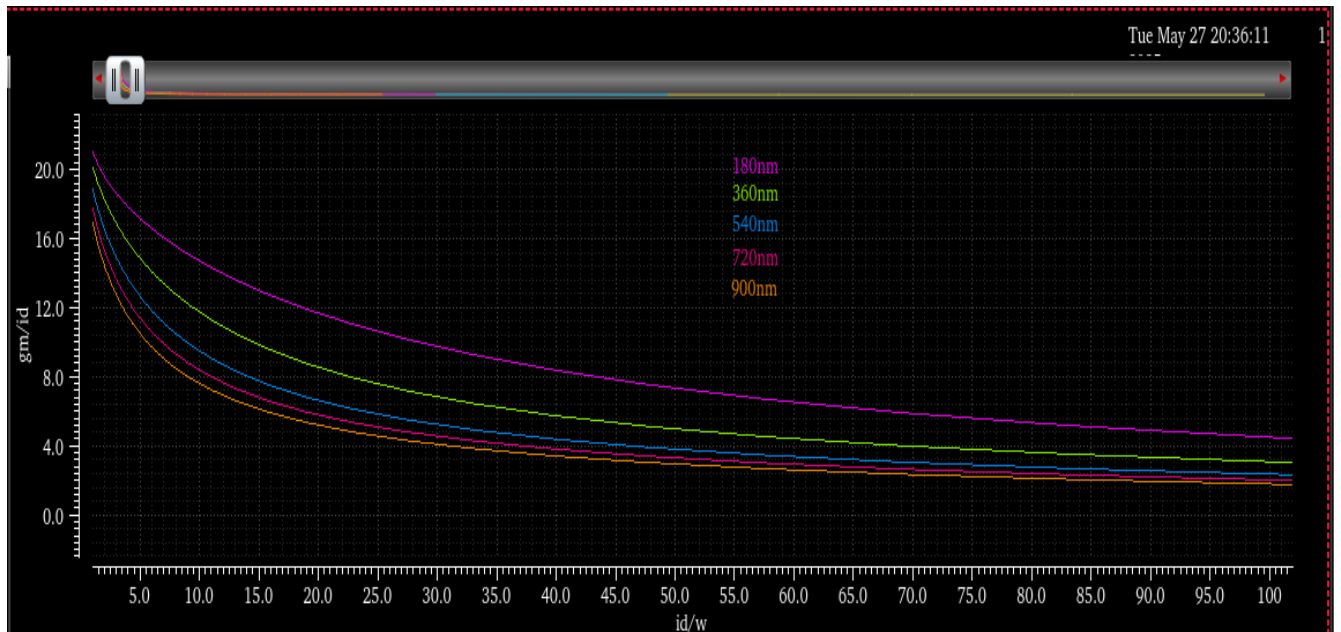

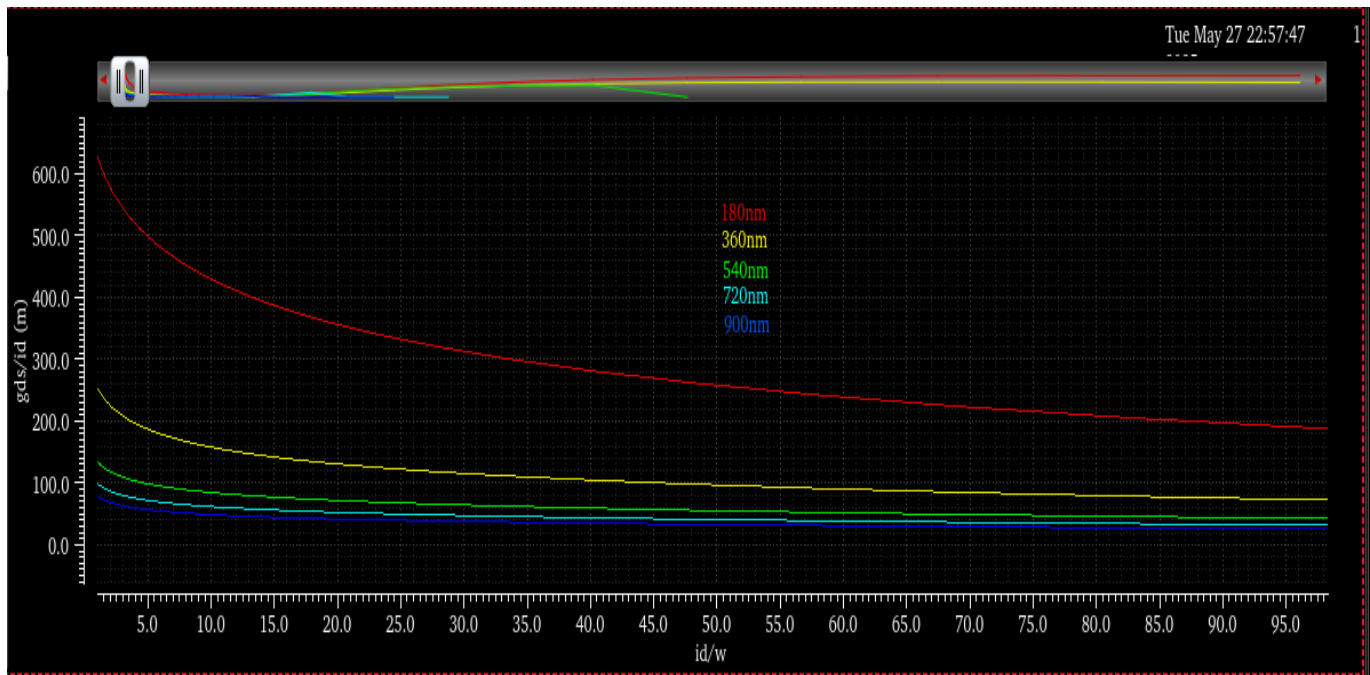


Out of these length I have chosen one( $l=540\text{nm}$ ) due to design requirements (I have explained in detail ahead).

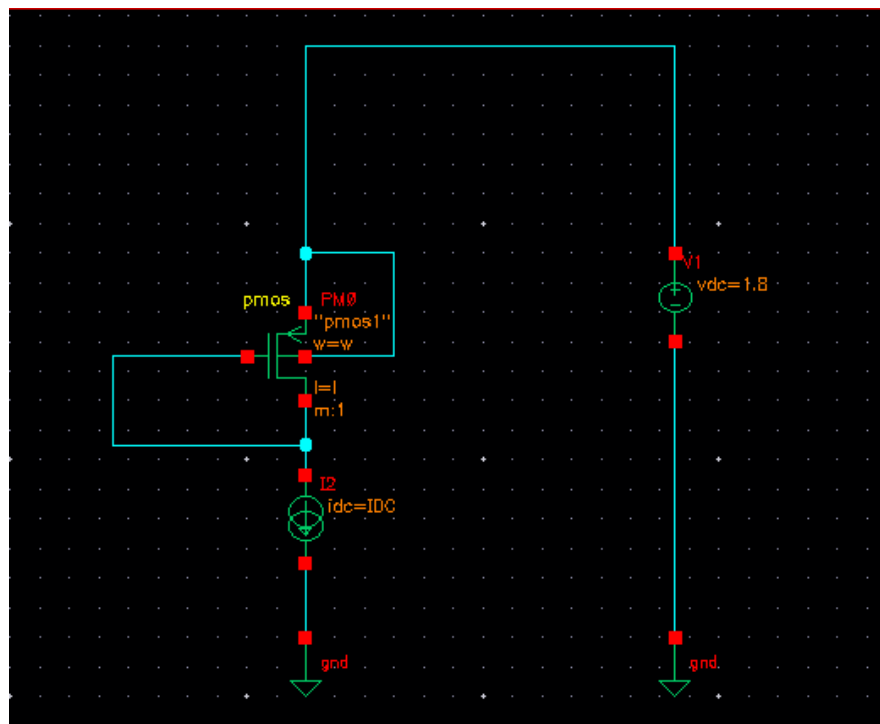Similarly, characterization of pMOS is also done.




# Transistor level Schematic

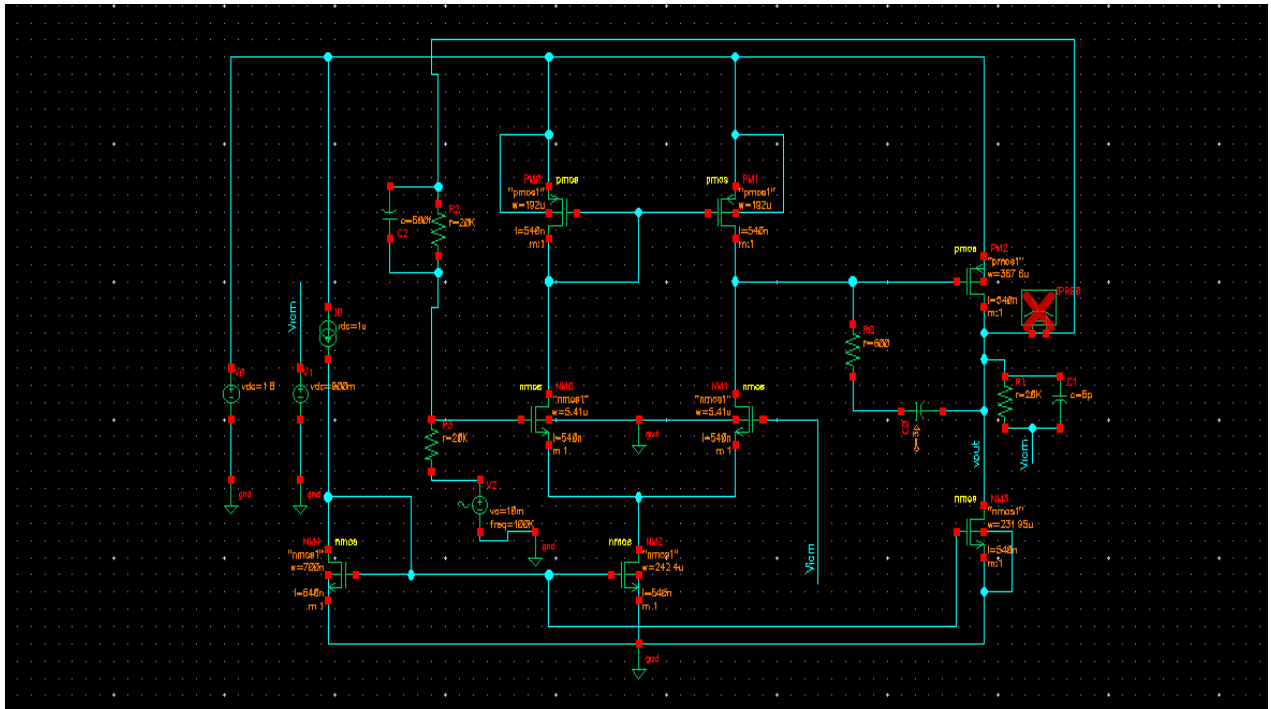

## Design Methodology
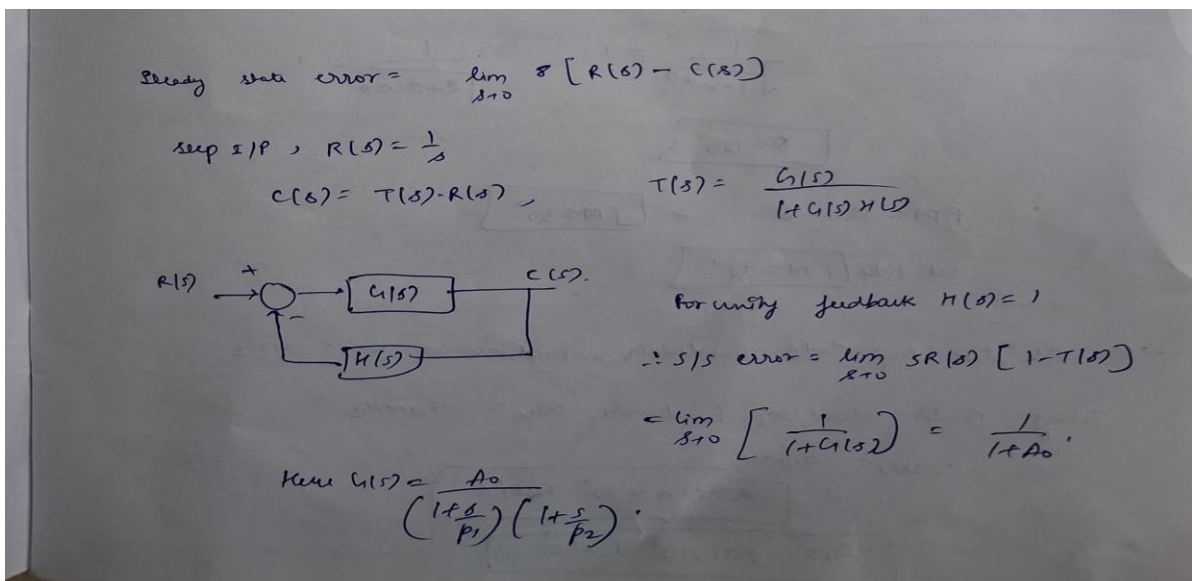
### Conditions for designing the circuit

- When the step input is applied to the closed loop system output must settle to the desired value with less than 0.1 % error.
- Closed loop frequency response must not exhibit any peaking.
- The closed loop 3dB bandwidth must be greater than 20MHz.



Given error  $< 0.1\%$

$$\therefore \frac{1}{1+A_0} < \frac{0.1}{100}$$

$$\frac{1}{1+A_0} < \frac{1}{1000}$$

$$\therefore A_0 > 1000$$

Assume

$$A_0 = 1500$$

For Phase Margin:

By Miller compensation, poles are far apart and it is acting as a first order system hence, at unity gain bandwidth loop gain has magnitude 1 @ a phase  $\theta$ .

$$\therefore LG = 1e^{j\theta}$$

$$\text{Close loop} = \frac{LG}{1+LG} = \frac{1e^{j\theta}}{1+1e^{j\theta}}$$

For no peaking,  $|\text{close loop}| \leq 1$

$$\therefore \left| \frac{1e^{j\theta}}{1+e^{j\theta}} \right| \leq 1$$

$$\frac{1}{\sqrt{1+e^{j2\theta}}} = 1 \Rightarrow \frac{1}{\sqrt{2+2\cos\theta}} = 1$$

$$\theta = 120^\circ$$

$$\therefore PM = 180 - \theta$$

$$\Rightarrow PM = 60^\circ$$

$$\text{let take } PM = 70^\circ$$

$\rightarrow$  Also, the close loop 3-dB Bandwidth, must not be  $< 20\text{MHz}$ .

Taking 3-dB closed loop bandwidth  $\omega_u = 40\text{MHz}$

$$\therefore \omega_u = 40\text{MHz}$$

$$= 40 \times 2\pi \times 10^6 \text{ Rad/s}$$

$$\omega_u = 2.51 \times 10^8 \text{ Rad/s}$$




$$\omega_u = \beta A_0 p_1$$

$$\omega_u = A_0 p_1$$

$$[\beta = 1, A_0 = 1500]$$

$$p_1 = \frac{\omega_u}{A_0} = \frac{2.51 \times 10^8}{1500} = 0.167 \times 10^6$$
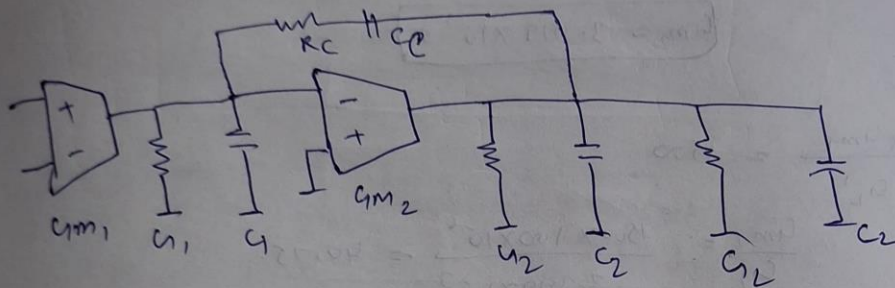
$$p_1 = 0.1675 \times 10^6 \text{ Rad/sec}$$



$$PM = 180 + [-90 - \tan^{-1}(\frac{\omega_u}{p_2})]$$

$$PM = 90 - \tan^{-1}(\frac{\omega_u}{p_2})$$

$$70 = 90 - \tan^{-1}(\frac{\omega_u}{p_2})$$

$$\frac{\omega_u}{p_2} = 0.3639$$

$$\therefore \omega_u = 0.3639 p_2 \Rightarrow p_2 = 6.9038 \times 10^8 \text{ rad/sec}$$

Gm values and the device sizes.

$$p_1 = \frac{C_1}{C_1 + C_c \left[ 1 + \frac{G_{m2}}{C_2'} \right]} = \frac{C_1}{C_c \frac{G_{m2}}{C_2'}}$$

$$p_2 = \frac{C_2' + G_{m2} \left[ \frac{C_c}{C_c + C_1} \right]}{C_2' + \frac{C_c C_1}{C_c + C_1}} = \frac{C_2' + G_{m2}}{C_2'}$$

assuming  $C_c \gg C_1$ ,  $C_2' \gg C_1$ ,  $C_c \gg C_2$ ,

$$C_2' \approx C_2 + C_{m2} \approx C_L = 5 \text{ pF}$$

$$C_L' = C_L + C_2$$

assume  $C_L = C_2$ ,  $C_L' = 2C_L = 2 \times C_L = 100 \times 10^6$

$$P_2 = \frac{C_L' + C_{m2}}{C_L'} \Rightarrow C_{m2} = P_2 C_L' - C_L'$$

$$= 6.9038 \times 10^8 \times 5 \times 10^{-12} - 100 \times 10^6$$

$$C_{m2} = 3.3519 \times 10^{-3} \text{ s}$$

$$A_0 = \frac{C_{m1} \times C_{m2}}{C_1 \times C_L'} = 1500$$

$$\frac{C_{m1}}{C_1} = \frac{1500 \times 100 \times 10^6}{3.3519 \times 10^{-3}} = 44.75$$

$C_L = C_2$  is chosen, as generally  $C_2$  has smaller value than  $C_L$   
 So by equating we get worst case scenario.

$$\omega_u = \frac{C_{m1}}{C_1} \times \frac{C_{m2}}{C_L'} \times \frac{C_L'}{C_c \times \frac{C_{m2}}{C_L'}}$$

$$\omega_u \approx \frac{C_{m1}}{C_c}$$

$$\omega_u = \frac{C_{m1}}{C_c}$$

assuming  $C_c = 3 \text{ pF}$   
 as  $C_c < C_L'$

$$C_{m1} = \omega_u \times C_c$$

$$= 2.513 \times 10^8 \times 3 \times 10^{-12}$$

$$C_{m1} = 7.54 \times 10^{-4} \text{ s}$$

$$A_0, \frac{C_{m1} \times C_{m2}}{C_1 \times C_L'} = A_0 \Rightarrow C_1 = \frac{C_{m1} \times C_{m2}}{A_0 \times C_L'} = \frac{7.54 \times 10^{-4} \times 3.35 \times 10^{-3}}{1500 \times 100 \times 10^6}$$

$$C_1 = 16.84 \mu\text{F}$$



Now  $g_{m1} = 7.54 \times 10^{-4} \text{ S} \approx 754 \mu\text{S}$

$C_{n1} = 16.84 \text{ pF}$


$g_{m2} = 3.35 \times 10^{-3} \text{ S}$

$C_{n2} = (50+50) \text{ pF} = 100 \text{ pF}$

$C_L = 5 \text{ pF}$

$C_c = 3 \text{ pF}$

$R_c = 300 \text{ ohms}$

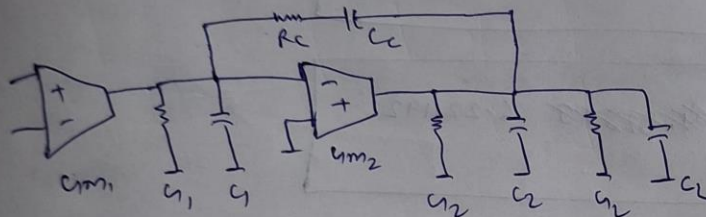

Now fixing  $w/L$  of all transistors.

# Stage-1

$$\frac{g_{m1}}{C_{n1}} = \frac{g_{m(m_1, m_2)}}{C_{dsn} + C_{dsp}} \quad (\text{assuming } C_{dsn} \approx C_{dsp})$$

$$\frac{g_{m1}}{C_{n1}} \approx \frac{g_{m(m_1, m_2)}}{2 C_{dsn}}$$

$$\frac{g_{m(m_1, m_2)}}{C_{dsn}} = 2 \times \left( \frac{g_{m1}}{C_{n1}} \right) = \frac{2 \times 7.54 \times 10^{-4}}{16.84 \times 10^{-6}}$$

$$\left( \frac{g_m}{C_{ds}} \right)_{m_1, m_2} = 89.55$$

Now, we will check which length is able to give this much of gain.

So, from graph, I got  $L = \boxed{540 \text{ nm}}$

So, for all transistors we fix  $L = \boxed{540 \text{ nm}}$

Using the look up table generated,

from the graph  $\frac{g_m}{g_{ds}} \approx \frac{2d}{W}$ , we got to know the value of  $\frac{2d}{W}$

$$\text{for } \frac{g_m}{g_{ds}} = 89.55$$

for  $\frac{g_m}{g_{ds}} = 89.55$ ,

we get  $\frac{I_D}{W} = \cancel{84.4464}$

22.387

now, we know  $\frac{I_D}{W}$  &  $\frac{g_m}{g_{ds}}$  from the graph of  $\frac{g_m}{g_{ds}}$  vs  $\frac{I_D}{W}$ , we can

know the value of  $\frac{g_m}{g_{ds}}$  corresponding to

$\frac{I_D}{W} = \cancel{84.4464}$  22.387

$\frac{g_m}{g_{ds}} = \cancel{8.22192}$  6.221192

$\left( \frac{g_m}{g_{ds}} \right)_{m_1, m_2} = \cancel{8.22192}$  6.221192

$(I_D)_{m_1, m_2} = \frac{(g_m)_{m_1, m_2}}{6.221192} = \frac{7.54 \times 10^{-4}}{\cancel{8.22192} \cdot 6.221192}$

$(I_D)_{m_1, m_2} = \cancel{121.2 \mu A}$

121.2  $\mu A$

Also,  $\left( \frac{I_D}{W} \right)_{m_1, m_2} = \cancel{84.4464}$  22.387

$(W)_{m_1, m_2} = \frac{(I_D)_{m_1, m_2}}{\cancel{84.4464} \cdot 22.387} = \frac{121.2 \mu A}{\cancel{84.4464} \cdot 22.387}$

$(W)_{m_1, m_2} = \cancel{5.41 \mu m}$

5.41  $\mu m$

5.41  $\mu m$

$W_{m_1} = \cancel{10.82 \mu m}$

$L_{m_1} = \cancel{850 nm}$

540 nm

$W_{m_2} = \cancel{10.82 \mu m}$  5.41  $\mu m$

$L_{m_2} = \cancel{850 nm}$  540 nm.



Now, for stage-2

$(g_m)_{m_2} \rightarrow$  Transconductance of PMOS  $m_2$

$$\frac{g_{m_2}}{C_{n2}'} = \frac{(g_m)_{m_2}}{2(2C_{ds})}$$

$$C_{n2}' = 2C_{n2}$$

$$C_{n2} = C_{ds1} + C_{ds2}$$

Assuming  $C_{ds1} = C_{ds2}$ .

$$\left(\frac{g_m}{C_{ds}}\right)_{P_{m_2}} = 4 \left(\frac{g_{m_2}}{C_{n2}'}\right)$$

$$\left(\frac{g_m}{C_{ds}}\right)_s = \frac{4 \times 3.35 \times 10^{-3}}{100 \times 10^{-6}} = 134.$$

now from  $\left(\frac{g_m}{C_{ds}}\right)_{P_{m_2}} = 134$ , length = ~~540 nm~~ 540 nm satisfies the gain condition.

from  $\frac{g_m}{C_{ds}}$  vs  $\frac{L_D}{W}$  graph we see which value of  $\frac{L_D}{W}$ ,  $\frac{g_m}{C_{ds}} = 134$ .

$$\rightarrow \text{so, for } \left(\frac{g_m}{C_{ds}}\right)_{P_{m_2}} = 134, \quad \boxed{\frac{L_D}{W} = 0.630095}$$

$$\rightarrow \text{Now from } \left(\frac{g_m}{L_D}\right) \text{ vs } \left(\frac{L_D}{W}\right), \text{ for } \frac{L_D}{W} = 0.630095$$

$$\text{we have } \frac{g_m}{L_D} = 14.443$$

$$\therefore \boxed{\left(\frac{g_m}{L_D}\right)_{P_{m_2}} = 14.443}$$

$$\therefore (L_D)_{m_2} = \frac{(g_m)_{m_2}}{14.443} = \frac{3.35 \times 10^{-3}}{14.443}$$

$$\boxed{(L_D)_{m_2} = 231.94 \text{ fA}}$$

$$\text{Also } \left(\frac{L_D}{W}\right)_{m_2} = 0.63096$$

$$\therefore \boxed{(W)_{m_2} = 367.6 \text{ fA}}, \quad \boxed{L_{m_2} = 540 \text{ nm}}$$

For no systematic offset

$$\left(\frac{2d}{w}\right)_{m3} = \left(\frac{2d}{w}\right)_{m4} = \left(\frac{2d}{w}\right)_{m5}$$

Also, we know that  $\left(\frac{2d}{w}\right)_{m5} = 0.63096$ .

$$(2d)_{m1} = (2d)_{m2} = (2d)_{m3} = (2d)_{m4} = 121.2 \text{ } \mu\text{A}.$$

$$\left(\frac{2d}{w}\right)_{m3} = 0.63096.$$

$$(w_{m3}) = \left(\frac{2dm3}{0.63096}\right) = 192 \mu\text{m}$$

$\therefore w_{m3} = 192 \mu\text{m}$	$w_{m4} = 192 \mu\text{m}$
$L_{m3} = 540 \text{ nm}$	$L_{m4} = 540 \text{ nm}$

Now, for  $m6, m7, m8$ .

$$\left(\frac{2d}{w}\right)_{m6} = \left(\frac{2d}{w}\right)_{m7} = \left(\frac{2d}{w}\right)_{m8}$$

$$\left\{ \begin{array}{l} (2d)_{m7} = 2(121.2) = 242.4 \mu\text{A} \\ 2d_{m8} = 231.95 \mu\text{A} \\ 2d_{m6} = 1 \mu\text{A} \end{array} \right.$$

Assuming  $(w)_{m6} = 1 \mu\text{m}$

then  $(w)_{m7} = 242.4 \mu\text{m}$

then  $(w)_{m8} = 231.95 \mu\text{m}$

$m6$
$w_{m6} = 1 \mu\text{m}$
$L_{m6} = 540 \text{ nm}$

$m7$
$w_{m7} = 242.4 \mu\text{m}$
$L_{m7} = 540 \text{ nm}$

$m8$
$w_{m8} = 231.95 \mu\text{m}$
$L_{m8} = 540 \text{ nm}$

## Loop gain (63.4798 dB)

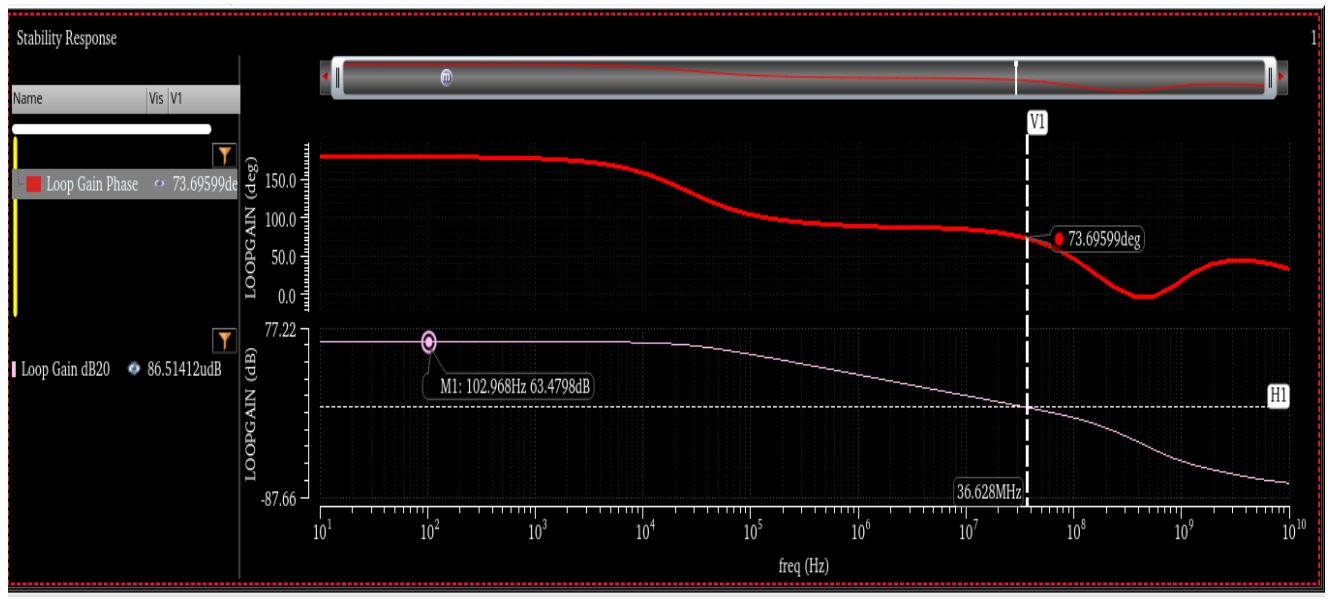


Fig: Simulated plot of loop gain magnitude and phase

## Phase Margin (74.004 deg)

Direct Plot Form

Plotting Mode: Append

Analysis:

☒ stb

Function:

☐ Loop Gain ☐ Stability Summary

☒ Phase Margin ☐ Gain Margin

☐ PM Frequency ☐ GM Frequency

Phase Margin = 74.0044 (Deg)

Add To Outputs ☐

Close Help